

3) $V_s = at + b$

$$5 = 150a + b$$

$$5 = 150a + b \rightarrow 50a = 5 \rightarrow a = 0,1$$

$$0 = 100a + b \rightarrow 0 = 100 \times 0,1 + b \rightarrow b = -10$$

$$\Rightarrow V_{S1} = 0,1t - 10 \quad (1)$$

$$2) a) i_1 = \frac{V_0}{R_1} \text{ car } V_d = 0.$$

$$i_2 = \frac{V_{S1}}{R_2}$$

$$b) i = i_1 + i_2 \text{ car } i = 0.$$

$$a(t+273) = \frac{V_0}{R_1} + \frac{V_{S1}}{R_2} \Rightarrow V_{S1} = R_2 a(t+273) - \frac{R_2}{R_1} V_0 \quad (2)$$

$$c) R_2 ? \quad R_1 = 10k\Omega$$

$$0,1 = R_2 a \rightarrow R_2 = \frac{0,1}{a} = \frac{0,1}{10^{-6}} = 10^5 \Omega$$

$$(0,1) \quad R_2 = 100k\Omega. \quad (1) \text{ et } (2) \Rightarrow -10 = R_2 a \times 273 - \frac{R_2}{R_1} V_0$$

$$-10 = 10^5 \times 10^{-6} \times 273 - 10 V_0$$

$$-10 = 27,3 - 10 V_0.$$

$$\rightarrow V_0 = \frac{27,3 + 10}{10} = 3,73V \quad (0,1)$$

II Pression 8/5

$$1) V_{S2} = ap + b$$

$$5 = 4 \times 10^5 a + b \rightarrow 5 = 2 \times 10^5 a \Rightarrow a = \frac{5}{2 \times 10^5}$$

$$(1) \quad V_{S2} = 2,5 \times 10^{-5} p - 5$$

$$0 = 2 \times 10^5 a + b \rightarrow a = 2,5 \times 10^{-5}$$

$$0 = 2 \times 10^5 \times 2,5 \times 10^{-5} + b \rightarrow b = -5$$

$$2) \frac{\Delta R}{R_0} = k_p; \quad k_p = 2,5 \times 10^{-8} Pa^{-1}$$

3) a) diviseur de tension

$$V_1 = \frac{R_0 + \Delta R}{2R_0} E \quad (1)$$

$$V_2 = \frac{R_0 - \Delta R}{2R_0} E \quad (2)$$

$$\rightarrow V_1 - V_2 = \frac{\Delta R}{R_0} E = k_p E \quad (0,5)$$

$$AN. \quad V_1 - V_2 = 2,5 \times 10^{-8} \times 4 \times 10^5 \times 10 = 0,1V \quad (0,5)$$

$$2) V_{S2} = 2,5 \times 10^{-5} p - 5 \quad \text{avec } p = \frac{V_1 - V_2}{k_p E} = \frac{V_1 - V_2}{2,5 \times 10^{-8} \times 10} = \frac{10^8 (V_1 - V_2)}{25} = 4 \times 10^6 (V_1 - V_2)$$

$$③ V_{S_2} = [A(V_2 - V_1) + V_r] \text{ avec } V_1 - V_2 = h\rho E \quad \text{compte n'importe} \quad \frac{2}{2}$$

$V_{S_2} = 10^2(V_1 - V_2) - 5 \quad (II)$

A.N. $E = 10V \rightarrow V_r = +5V \quad (I)$

$A = +10^2$

B] CHAÎNE DE COMMANDE

III]. Moteur 4 pôles. $E' = h m \Phi$

1 ① $I_e = \dot{\theta} \rightarrow \Phi = \dot{\theta} \rightarrow E' = k_m \quad E'_N = U_N - R I'_N = 170 - 4,2 \times 2,6$

$k = \frac{E'}{m} \quad E'_N = 170 - 10,92 \approx 159V \quad (159,08)$

et $m_N = 50 \text{ tr/s} \rightarrow k = 3,18 \text{ Vs} \text{ rad}^{-1}$

1 ② $C_e = \frac{EI}{2\pi m} = \frac{KI}{2\pi}$

1 ③ $C_{eN} = \frac{K I_N}{2\pi} = 3,18 \times \frac{2,6}{2\pi} = 1,317 \text{ Nm} \quad (1,31655)$

1 $C_{uN} = \frac{P_{uN}}{2\pi m_N} = \frac{368}{2\pi \times 50} = 1,171 \text{ Nm} \quad (1,17138)$

IV]. Variateur et sa commande (4 pôles)

(4,5) $u_c = 10V \rightarrow \theta = 180^\circ \quad \theta = h' u_c \quad U = 220V \quad 50Hz$

① a) $v = E' + Ri + L \frac{di}{dt}$ b) $V_{moy} = E' + RI_{moy} + 0$

1 c) $V_{moy} = k_m + RI_{moy} \rightarrow m = \frac{V_{moy} - RI_{moy}}{k}$

0,5 ② AN $m = \frac{170 - 4,2 \times 2,6}{3,18} = 28 \text{ tr/s}$

③ $u_c = h' N_D \quad N_D = 255 \rightarrow u_{cmax} = 9,96V \Rightarrow h' = \frac{9,96}{255}$

0,5 a) $(S) = 00111111 = 63$

0,5 b) $u_c = h' \times N_D = \frac{9,96}{255} \times 63 = 2,46V$

et $\theta = h' u_c \text{ avec } \theta = 180^\circ \text{ rad} \quad u_c = 10V \rightarrow h' = \frac{180}{10} = 18^\circ \text{ V}^{-1}$

0,5 $\theta = 18 \times 2,46 = 44,3^\circ$